

## Circuits

Investigating <sup>conductors</sup> motion of electrons  
(idealized)  
in metals in ways that do  
useful work.

Reminder for a charged particle


$$PE(\vec{r}) = q \underbrace{V(\vec{r})}$$

electric potential  
at that location

If  $V(\vec{r})$  changes as  $\vec{r}$  changes  
then  $q$  will feel a force in direction  
of lower PE

$$\vec{F} = -\vec{\nabla} PE$$

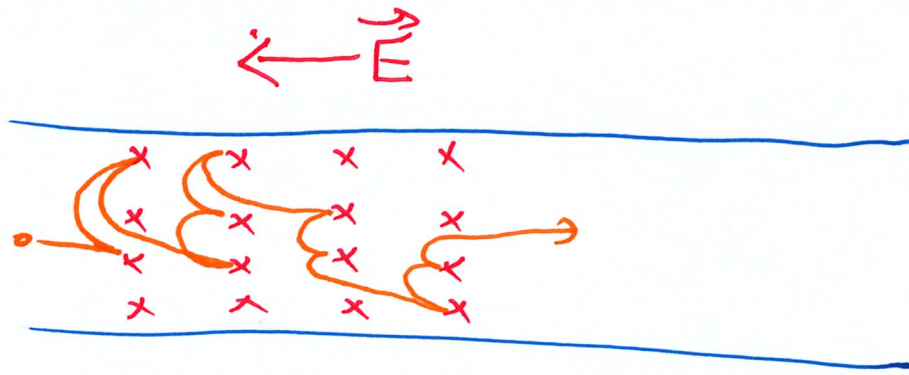As  $q$  moves towards lower  
PE,  $\vec{F}$  does work on it  
Expect KE to increase




Electron collided with individual atoms ; interact via coulomb force  $\Rightarrow$  elastic collision  
 $\Rightarrow$  Same KE gets transferred to atoms in material

(Effect: Heats up  $\frac{1}{2}P_{III}$  average KE related to temp)

Turns out that speed of conduction electrons is relatively constant so work done on electrons by force ends up either heats things or does mechanical work.

When I talk about current

$$I = \int \vec{J} \cdot d\vec{A}$$

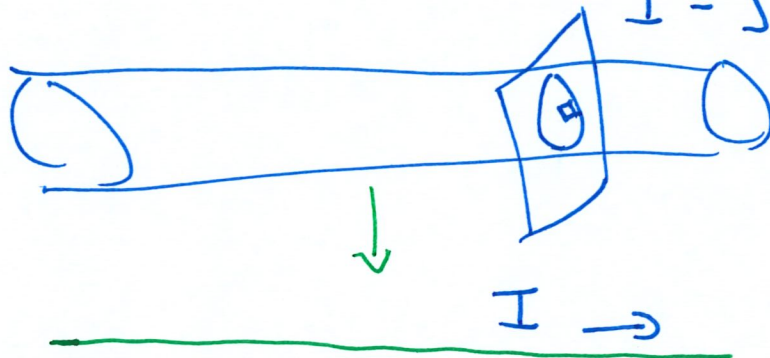

$$A \sim r^2$$

model as line

Current = total charge per time  
moving along line  
direction: Way positive  
charges would move

---

Any place where  $q$ 's do work  
"resistor"



PE decreases  
Does work

All wires assume charges  
move along wires unimpeded.



## 12-2-Example- DC circuits1

### DC circuits - I

An electron moves from a location where it is at potential  $1V$  to a place where it is at potential  $3V$ .

- What is the change in the electron's potential energy?
- Assuming the electron's kinetic energy has not changed, how much work did the electron do?


$$\begin{aligned}\text{Know } PE &= qV \\ \Delta PE &= qV_f - qV_i \\ &= q(V_f - V_i) \\ &= (-1.6 \times 10^{-19} \text{ C})(3V - 1V) \quad 1V = 1J/C \\ &= -3.2 \times 10^{-19} \text{ J}\end{aligned}$$

$$\Delta KE + \Delta PE = W_{N \text{ on Electron}}$$

$$0 + (-3.2 \times 10^{-19} \text{ J}) = W_{N \text{ on Electron}}$$

Electron has done  $-W_{N \text{ on electron}}$   
or  $3.2 \times 10^{-19} \text{ J}$  of work

How electric power is actually generated

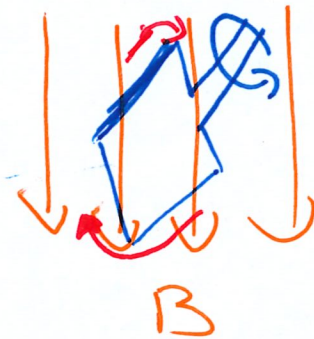


A current carrier is moved in the presence of a magnetic field; charged particles feel a force, which does work on them, increasing their P.E.

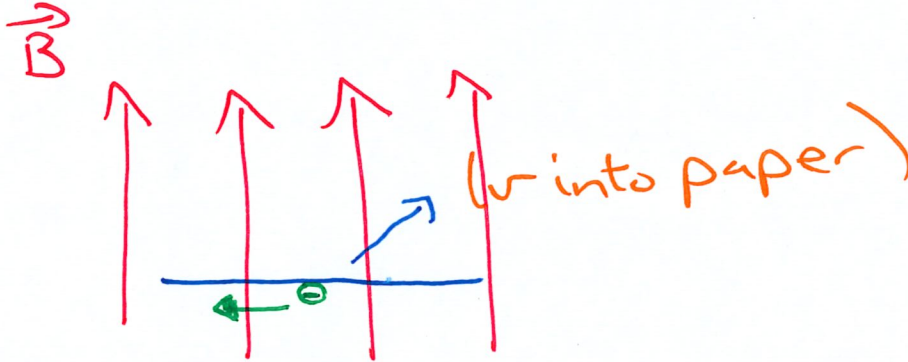
## DC circuits - II

A  $1.5\text{m}$  long piece of metal is oriented in the  $x$ -direction. It is moved with a velocity  $20\frac{\text{m}}{\text{s}}\hat{j}$  in a region where the magnetic field is  $0.4\text{T}\hat{k}$ .

How much work would be done on an electron by the Lorentz force as it moves from one end of the metal to the other?


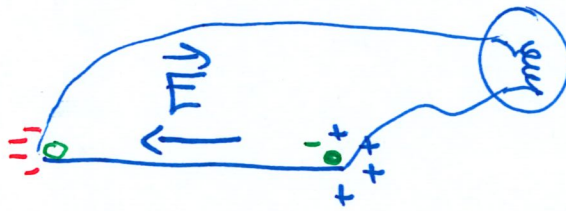
$$\begin{aligned}\vec{F} &= q\vec{v} \times \vec{B} \\ &= (-1.6 \times 10^{-19} \text{ C}) (20 \text{ m/s } \hat{j}) \times (0.4 \text{ T } \hat{k}) \\ &= -1.28 \times 10^{-18} \text{ N } \hat{i}\end{aligned}$$



B/c of charge separation there is an  $\vec{E}$ , so potential difference

$$\begin{aligned} W &= \vec{F} \cdot \Delta \vec{r} \\ &= (-1.28 \times 10^{-18} \text{ N} \hat{z}) \cdot (-1.5 \text{ m} \hat{z}) \\ &= 1.92 \times 10^{-18} \text{ J} \end{aligned}$$


Similar way of saying

$$\begin{aligned} \Delta PE &\rightarrow q \Delta V \\ &(-1.6 \times 10^{-19} \text{ C})(-12 \text{ V}) \end{aligned}$$

Charge separation  $\rightarrow$   $V$  not constant



Resistors:

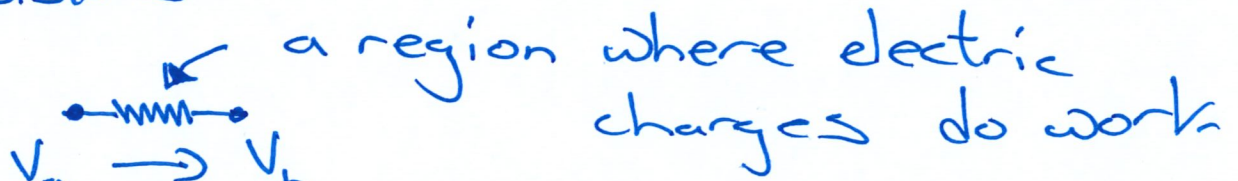

$$\Delta V = V_B - V_A = -IR$$

↑ resistance  $\Omega$

$$1\Omega = 1V/A$$

$$= 1Vs/C$$

$$= 1Js/C^2$$

A positive charge moving in direction  $I$  will have its potential decreased by  $IR$

Multiple resistors / resistive elements




$$V_B - V_A = -R_1 I$$

$$V_C - V_B = -R_2 I$$

$$\begin{aligned} V_C - V_A &= V_C - V_B + V_B - V_A \\ &= -R_2 I + (-R_1 I) \\ &= -(R_1 + R_2) I \end{aligned}$$


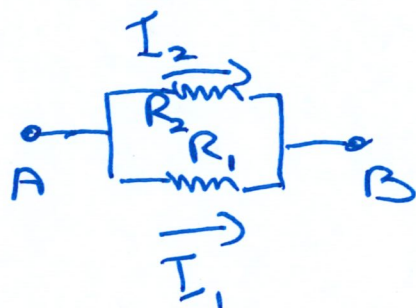
$$R_{eq} = R_1 + R_2 \quad (\text{in series})$$



$$V_B - V_A = -I_1 R_1$$

$$V_B - V_A = -I_2 R_2$$

as well

$$\text{Total through both} = I_1 + I_2$$

$$\rightarrow V_B - V_A = -(I_1 + I_2) R_{eq}$$

How do we work out  $R_{eq}$

Want it as a function of  $R_1$  &  $R_2$

$$\text{Know } I_1 R_1 = I_2 R_2 = -(V_B - V_A)$$

$$\left( I_1 = \frac{-(V_B - V_A)}{R_1} \quad I_2 = \frac{-(V_B - V_A)}{R_2} \right)$$

$$V_B - V_A = \left[ \frac{-(V_B - V_A)}{R_1} + \frac{-(V_B - V_A)}{R_2} \right] R_{eq}$$

$$1 = \left[ \frac{1}{R_1} + \frac{1}{R_2} \right] R_{eq}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \quad (\text{in parallel})$$

Ohm's law says that current density  $\vec{J}$  is proportional to  $\vec{E}$


$$\vec{J} = \sigma \vec{E}$$

"conductivity"

depends on material



Small wire  
~ smaller  
current

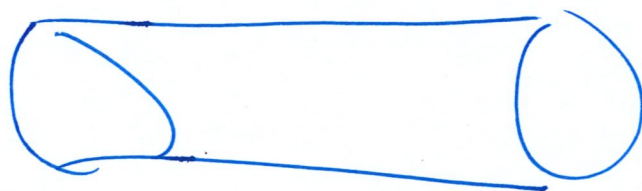

thick wire  
~ bigger  
current

$$\text{Electric Field} \sim \frac{d}{dx} V \sim \frac{\Delta V}{l}$$